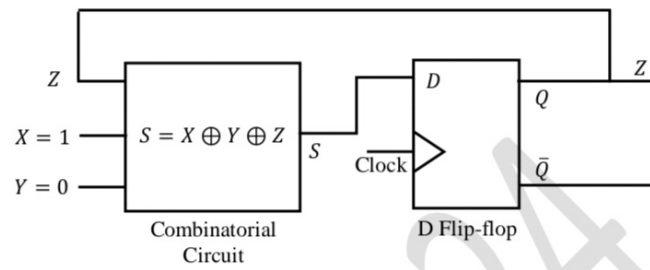


1. In the circuit, the present value of Z is 1. Neglecting the delay in the combinational circuit, the values of S and Z , respectively, after the application of the clock will be



- (a) $S = 0, Z = 0$
- (b) $S = 0, Z = 1$
- (c) $S = 1, Z = 0$
- (d) $S = 1, Z = 1$